

### 3. Introduction to the Nexys 4 FPGA Board:

Please review Nexys 4 details from your first week of lab/lecture material [dir pdf pdf .avi](#).

### 4. FPGA Design Flow:

Please refer to your first week's lab on Nexys 4: Xilinx\_project\_synthesis\_on\_Vivado [.pdf](#) [.mp4](#)

### 5. Prelab: (Refer to the first paragraph of [nexys4\\_rm.pdf](#) for the first two questions)

Q 5. 1: Circle the family and device category of the FPGA used on Nexys4 board? (1pt)

7 Series		UltraScale		UltraScale+	
Spartan-7	Artix-7	Kintex UltraScale	Virtex UltraScale	Kintex UltraScale+	Virtex UltraScale+
Kintex-7	Virtex-7				

Q 5. 2: Google “CSG324 @Xilin.com” and find what is CSG324 in the part number of the device used on Nexys-4? (1pt)

☐ Speed grade ☒ Package ☐ Serial number ☐ Model number

Q 5. 3: The **state memory** is usually implemented using: (2pts)

☐ And-Or gates  
☐ RAM  
☒ flip-flops  
☐ latches

Q 5. 4: We will implement the detour signal controller using One-Hot state assignment method. How many D-flip-flops are needed to implement the controller? (2pts)

On power-on reset (i.e when power is first applied to the system), how many Flip-Flops are preset? 1 (1pt) and how many are cleared? 8 (1pt)

In the schematic ee254l\_detour.sch (on page 11), next state logic for which state(s) is complete? (2pts)

IDLE, L12, L123

Next State Logic (NSL) is purely a combinational  
 (combinational/sequential) circuit. (2pts)

Output Function Logic (OSL) is purely a combinational  
 (combinational/sequential) circuit. (2pts)


Q 5. 5: Refer to the figure on the right, reproduced from this [pdf](#), suggesting a way to display the output of a 16-bit binary number as a 4-digit hexadecimal number going from 0000 to FFFF on the 4 SSDs of a Nexys-3 board.

Name the three components and also state whether it is a combinational logic or a sequential logic.

1. 2/4 Decoder (combinational)
2. 4/1 mux (combinational)
3. Hex to SSD converter (combinational)

Now, if we want to display the output of a 32-bit binary counter as an 8-digit hexadecimal number going from 0000 0000 to FFFF FFFF on the 8 SSDs of a Nexys-4 board, what three components you intend to use?

 1. 3/8 Decoder
2. 4bit wide 8/1 mux
3. Hex to SSD converter



Do you believe that one of the above two displays is brighter. Yes / No.


If you said "Yes", then which is brighter? A (A/B).

A= 16-bit counter display on the 4 digits of Nexys-3, B= 32-bit counter display on the 8 digits of Nexys-4


Why? Because the frequency is higher

Q 5. 6: In the above diagram, VCC (= 3.3 volts = a constant logic 1) was tied inside the FPGA to the DP (via pin M13) to make all (one dot point all dot points) continuously off (to be on to be off).

 Q 5. 7: Though we do not perform fractional arithmetic needing to display a dot point (such as the dot point in 23.42 or 1.234) in this course, it is possible to do so as the so called SSDs (Seven Segment Displays) contain actually 8 segments per digit including the dot point.



 In a revised detour lab, suppose that you are given a Nexys-3 board with all singular LEDs removed. You are asked to use the four dot points on the 4 SSDs to represent the 4 groups of lights, GL, G1, G2, and GR. Show (on the side) **the needed additions** to control pin M13 in the figure in the above Q 5.5 to achieve this.



## 7. Lab Report:



Name: \_\_\_\_\_ Date: \_\_\_\_\_  
 Lab Session: \_\_\_\_\_ TA's Signature: \_\_\_\_\_

**For TAs:** Pre-lab (10): \_\_\_\_\_ Schematic completion (70): \_\_\_\_\_ Report (out of 20): \_\_\_\_\_


Comments:

  - Q 7. 1: Refer to Xilinx [UG616](#). What are the two different D-flip-flops that are used in this lab? What is the difference between them? (2pts)  
*FDP (output High when power applied)*  
*FDC (output low when power applied)*
- Q 7. 2: Name 2 more D-flip-flops that are available in the Xilinx library [UG616](#) (and have enable pins) and briefly explain how are they different from the ones that are used in this lab. (8pts)  
*FDR (set output low on positive clock edge)*  
*FDS (set output High on positive clock edge)*
- Q 7. 3: Which pin of the FPGA is connected to the **BtnC** on the Nexys 4 board? Refer to the reference manual for the Nexys 4 or the .xdc file of Nexys 4 (see files in the [dir](#)). (4pts)  
*E16*
- Q 7. 4: Which three special buffers are needed for signals that connect to the input and output devices (including the on-board clock generator)? Give their names and whether they are needed to connect inputs or outputs or both. (6pts)  
*BUFGP (Both)*  
*DBUF (Output)*  
*IBUF (Input)*
- Q 7. 5: The frequency of the clock entering the FPGA is 100MHz. Notice that we are dividing the input clock by using counters. Calculate the frequency of the divided clock (DIVCLK[25]) that triggers the detour signal state machine. (5pts)  

$$\frac{100\text{MHz}}{2^{26}} = 1.49 \text{ Hz}$$
- Q 7. 6: Here, L (for Left) and R (for Right) are always opposite to each other. Can you optimize (simplify) the 4-bit output  $R_0 R_1 R_2 R_3$  generating combinational logic on the side? Try to avoid the expensive 4-bit wide 2-to-1 mux by tying either VDD or GND or L or R as appropriate to each of the four outputs. Note: Since  $R = \sim L$ , instead of generating  $L_{\text{Bar}}$  by inverting L, you can use R wherever you need  $L_{\text{Bar}}$ .
- Based on the above, you suggest that you could have avoided *mux 8 bit 2x1*  
*8-bit wide 2-to-1 mux*  
 in the second page of the top schematic.






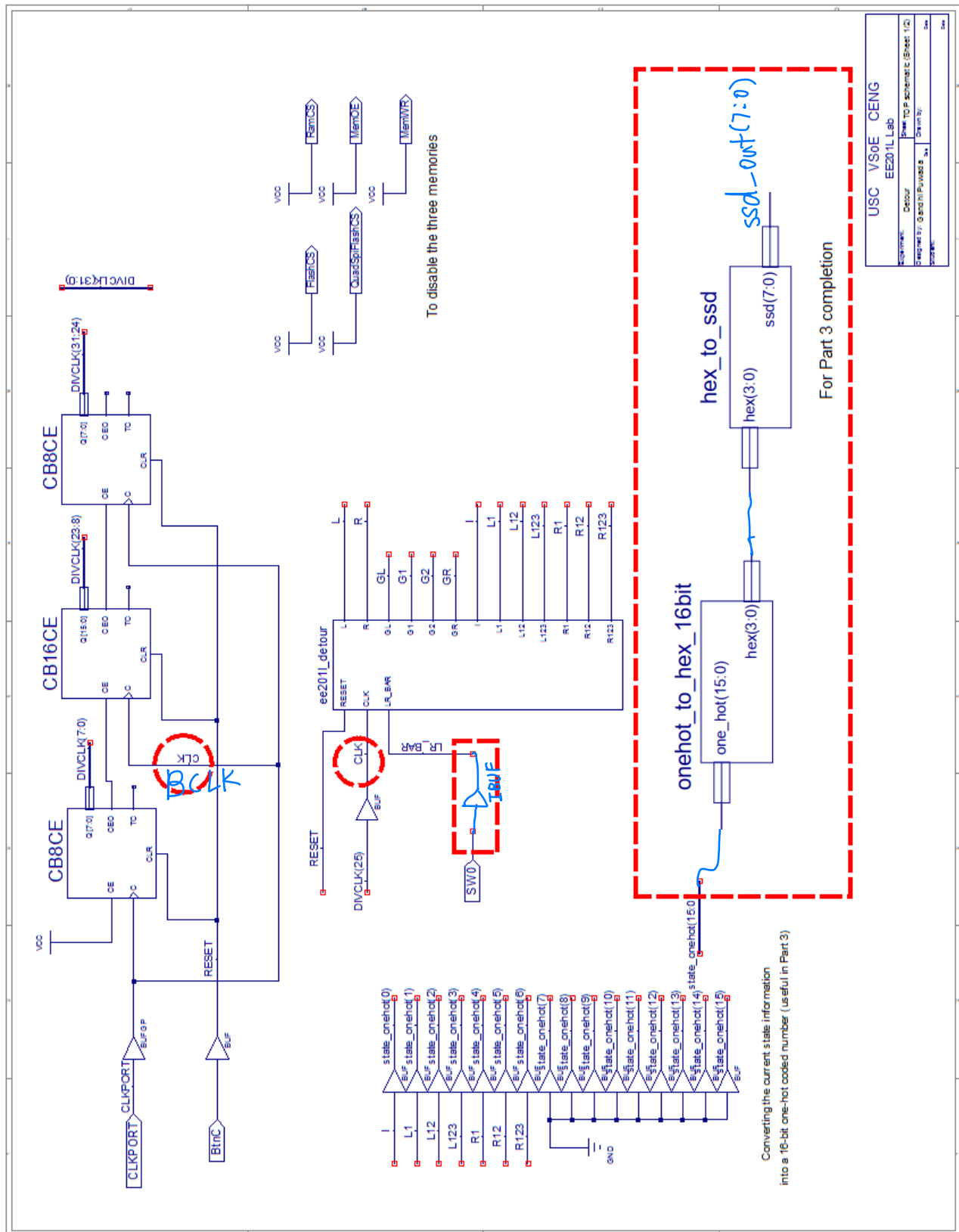



 
### Part 3 On this page generate only Anode and Cathode controls.

**Method #1:** Permanently disable **AN1** and **AN2**. Then activate **AN0** and **AN3** alternately at a reasonable speed (*neither too fast nor too slow*, your TA will help) while sending the correct 7-segment (actually 8-segment) signals (**Ca-Cg**) to the SSDs. You need a 8-bit wide 2-to-1 mux for this. You might use **DIVCLK (15)** to alternately enable one of **SSD0** or **SSD3** to accomplish this.



**Method #2:** Instead of permanently disabling **AN1** and **AN2** (as in Method#1), let us send **Ca-Cg, Dp=11111111** to the 8 cathodes (remember these are active low so this will blank the displays). Now we need to activate the 4 anodes, one at a time in sequence, while sending the corresponding 8-segment information to the cathodes with a 8-bit wide 4-to-1 mux. You can use perhaps **DIVCLK (15 : 14)** for this purpose.

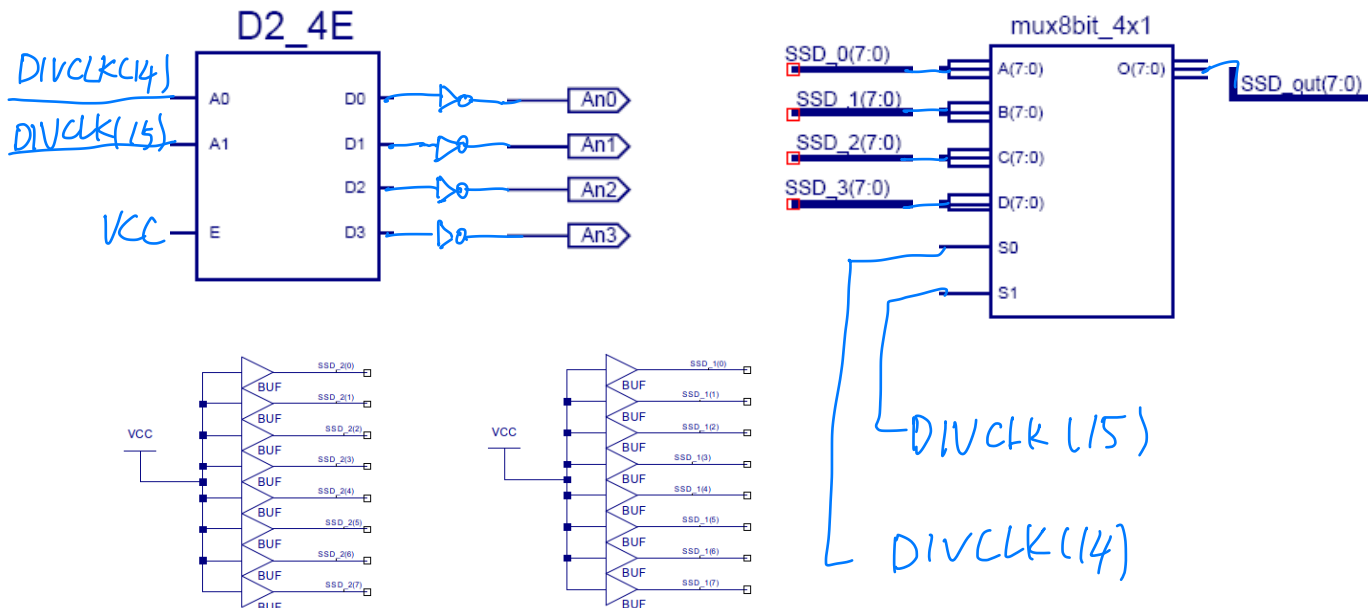

You can use a 2x4 decoder such as the above **D2\_4E**. Look up the Xilinx library [UG616](#) for the **D2\_4E** decoder to check if the enable input is active high or low and the outputs are active high or active low. We also provided you with the 8-bit wide 4x1 mux shown above. The diagrams on pages 18/29 to 20/29 (section 9.1 on Seven Segment Display) of the Nexys 4 reference manual will help you in understanding the scanning operation. **Celebrate the completion of your lab!**